 
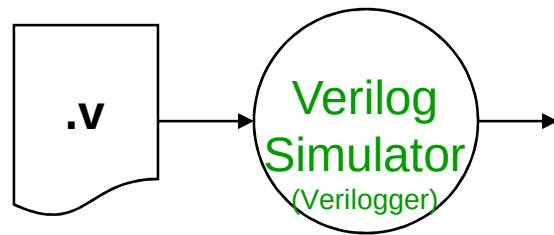

Esercitazione 1

Verilog e MIPS

<http://www.dii.unisi.it/~giorgi/didattica/arcad1>

All figures from Computer Organization and Design: The Hardware/Software Approach, Second Edition, by David Patterson and John Hennessy, are copyrighted material. (COPYRIGHT 1998 MORGAN KAUFMANN PUBLISHES, INC. ALL RIGHTS RESERVED.) Figures may be reproduced only for classroom or personal educational use in conjunction with the book and only when the above copyright line is included. They may not be otherwise reproduced, distributed, or incorporated into other works without the prior written consent of the publisher.

Verifica Logica



File Verilog

Diagramma Temporale


Istallazione di Verilogger

- Distribuibile gratuitamente
- Istruzioni per l'istallazione sul proprio PC (Windows)
 - <http://www.dii.unisi.it/~giorgi/didattica/tools/verilog.exe>
 - Eseguire (scompatta in C:\VERILOG)
 - Crearsi un link (es. dal Desktop) al file C:\VERILOG\vlogev.exe
- Nel Laboratorio
 - Individuare l'icona relativa




Uso di Verilogger: un primo esempio

 - Lanciare il programma Verilogger (vlogev.exe)
 - Selezionare nella prima finestra "VeriLogger"





Verillogger: schermata iniziale


 


- Sono presenti 4 finestre
 - Report
 - Project
 - Parameter
 - Diagram



Selezione/Creazione di un progetto

  


 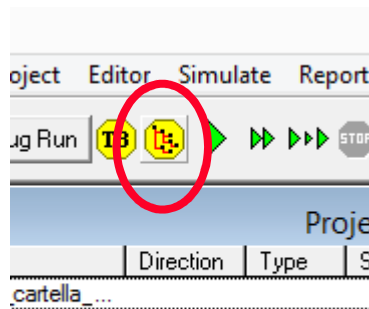Compilazione e generazione del diagramma temporale



```
Report - verilog.log
Finished Phase II
Entering Phase III...
C:\Users\Roberto\Desktop\verilog_cartella_pulita\prova.v: L10: warning: Port sizes don't match in port #3
C:\Users\Roberto\Desktop\verilog_cartella_pulita\prova.v: L10: warning: Port sizes don't match in port #4
Finished Phase III
Highest level modules: syncad_top
Finding handle to syncad_top.TopLevel.reset_
Finding handle to syncad_top.TopLevel.clock
Finding handle to syncad_top.TopLevel.X
Finding handle to syncad_top.TopLevel.Y
Finding handle to syncad_top.TopLevel.rfd
Finding handle to syncad_top.TopLevel.dav_
Finding handle to syncad_top.TopLevel.q
Finding handle to syncad_top.TopLevel.done
Finding handle to syncad_top.TopLevel.STAR
Compile Complete
```

  

 

Porta nand


```
`timescale 1ns / 1ps
//create a NAND gate out of an AND and an Inverter
module some_logic_component (c, a, b);
    // declare port signals
    output c;
    input a, b;
    // declare internal wire
    wire d;
    //instantiate structural logic gates
    and a1(d, a, b); //d is output, a and b are inputs
    not n1(c, d);    //c is output, d is input
endmodule

//test the NAND gate
module test_bench; //module with no ports
    reg A, B;
    wire C;

    //instantiate your circuit
    some_logic_component S1(C, A, B);

    //Behavioral code block generates stimulus to test circuit
    initial
    begin
        A = 1'b0; B = 1'b0;
        #50; $display("A = %b, B = %b, NAND output C = %b \n", A, B, C);
        A = 1'b0; B = 1'b1;
        #50 $display("A = %b, B = %b, NAND output C = %b \n", A, B, C);
        A = 1'b1; B = 1'b0;
        #50 $display("A = %b, B = %b, NAND output C = %b \n", A, B, C);
        A = 1'b1; B = 1'b1;
        #50 $display("A = %b, B = %b, NAND output C = %b \n", A, B, C);
    end
endmodule
```

NAND: diagramma e report

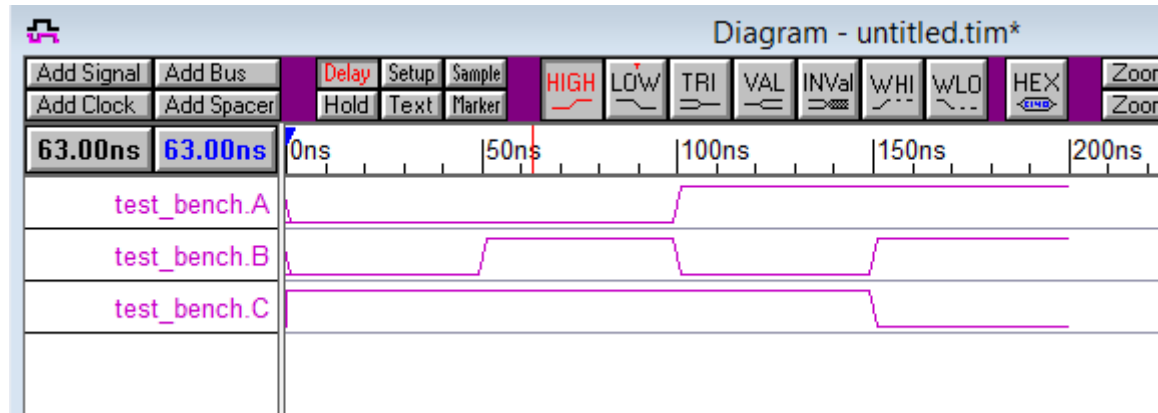


Report - C:\VERILOG\verilog.log

```
Finding handle to syncad_top.test_bench.C
Compile Complete
.
Running...
A = 0, B = 0, Nand output C = 1
A = 0, B = 1, Nand output C = 1
A = 1, B = 0, Nand output C = 1
A = 1, B = 1, Nand output C = 0

0 Errors, 0 Warnings
Compile time = 0.02000, Load time = 0.28400, Execution time = 0.02400
```


Documentazione

 

 ESEMPIO: COSTRUZIONE DEL DATAPATH DEL MIPS


Costruzione del Datapath

Gestione indirizzo istruzione successiva I segnali di controllo vengono pilotati in base a "op-code" e "funct" dell'istruzione:



Gestione del risultato della ALU o dato dalla memoria

Datapath piu' preciso

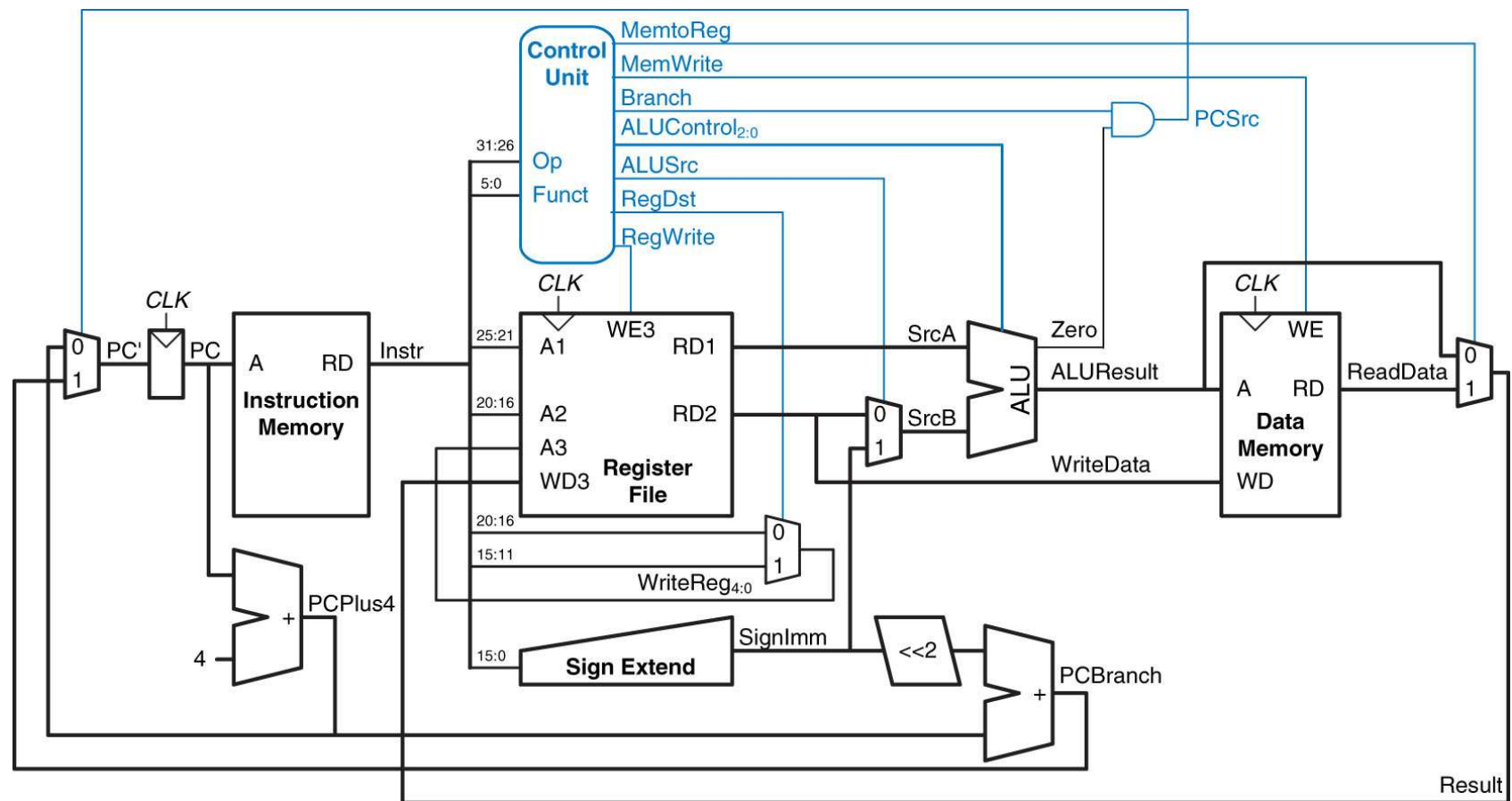

RegWrite
PCSrc
ALUSrc
AluControl[2:0]
MemWrite
MemtoReg


MemRead

Non c'e'

Branch
RegDst

Nuovi

MIPS processor

 

```
module mips(clk, reset, readdata, instr
    pc, memwrite, aluout, writedata);
input clk, reset;
input [31:0] readdata;
input [31:0] instr;
output [31:0] pc;
output memwrite,
output [31:0] aluout, writedata;
```

```
wire memtoreg, alusrc, regdst,
    regwrite, pcsrc, zero;
wire [2:0] alucontrol;
```

```
controller c(instr[31:26], instr[5:0], zero,
    memtoreg, memwrite, pcsrc,
    alusrc, regdst, regwrite,
    alucontrol);
```

```
datapath dp(clk, reset, memtoreg, pcsrc,
    alusrc, regdst, regwrite,
    alucontrol,
    zero, pc, instr,
    aluout, writedata, readdata);
```

```
endmodule
```

MIPS Controller

```
module controller(opcode, funct, zero,
  zero, memtoreg, memwrite, pcsrc, alusrc,
  regdst, regwrite, alucontrol);

input [5:0] opcode, funct;
input zero;
output memtoreg, memwrite;
output pcsrc, alusrc;
output regdst, regwrite;
output [2:0] alucontrol;


wire [1:0] aluop;
wire branch;

maindec md(opcode, memtoreg, memwrite, branch,
  alusrc, regdst, regwrite, aluop);

aludec ad(funct, aluop, alucontrol);

assign pcsrc = branch & zero;

endmodule
```

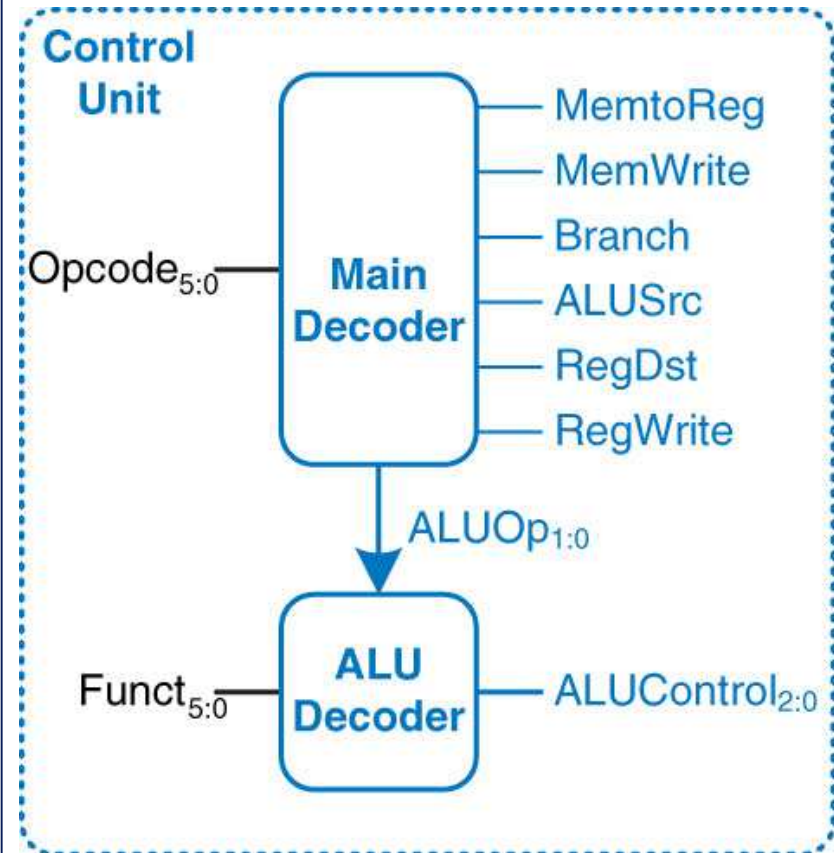


Main Decoder

```
module maindec(opcode, memtoreg, memwrite,
  branch, alusrc, regdst, regwrite, aluop);

input [5:0] opcode;
output memtoreg, memwrite;
output branch, alusrc;
output regdst, regwrite;
output [1:0] aluop;

wire [7:0] controls;
assign {regwrite, regdst, alusrc, branch, memwrite,
  memtoreg, aluop} = controls;

 always @(opcode)
  case(opcode)
    6'b000000: controls <= 8'b11000000; // RTYPE
    6'b100011: controls <= 8'b10100100; // LW
    6'b101011: controls <= 8'b00101000; // SW
    6'b000100: controls <= 8'b00010001; // BEQ
    6'b001000: controls <= 8'b10100000; // ADDI
    default: controls <= 8'bxxxxxxxx; // illegal op
  endcase
endmodule
```




ALU Decoder

```
module aludec(funct, aluop,  alucontrol);

input [5:0] funct,
input [1:0] aluop,
output [2:0] alucontrol;

always @(aluop)
case(aluop)
  2'b00: alucontrol <= 3'b010; // add (for lw/sw/addi)
  2'b01: alucontrol <= 3'b110; // sub (for beq)
  default: case(funct) // R-type instructions
    6'b100000: alucontrol <= 3'b010; // add
    6'b100010: alucontrol <= 3'b110; // sub
    6'b100100: alucontrol <= 3'b000; // and
    6'b100101: alucontrol <= 3'b001; // or
    6'b101010: alucontrol <= 3'b111; // slt
    default: alucontrol <= 3'bxxx; // ???
  endcase
endcase
endmodule
```

 

MIPS Datapath

Nota: I seguenti esempi vanno adattati alla sintassi Verilog !

```
module datapath(input clk, reset, input memtoreg, pcsrc, input alusrc, regdst, input regwrite, jump,
                input [2:0] alucontrol, output zero, output [31:0] pc, input [31:0] instr, output [31:0] aluout,
                writedata, input [31:0] readdata);

wire [4:0] writereg; wire [31:0] pcnext, pcnextbr, pcplus4, pcbranch; wire [31:0] signimm, signimmsh;
wire [31:0] srca, srcb; wire [31:0] result;

// next PC logic
flopr #(32)  pcreg(clk, reset, pcnext, pc);
adder       pcadd1(pc, 32'b100, pcplus4);
sl2         immsh(signimm, signimmsh);
adder       pcadd2(pcplus4, signimmsh, pcbranch);
mux2 #(32)  pcbrmux(pcplus4, pcbranch, pcsrc, pcnextbr);
mux2 #(32)  pcmux(pcnextbr, {pcplus4[31:28], instr[25:0], 2'b00}, jump, pcnext);

// register file logic
Regfile     rf(clk, regwrite, instr[25:21], instr[20:16], writereg, result, srca, writedata);
mux2 #(5)   wrmux(instr[20:16], instr[15:11], regdst, writereg);
mux2 #(32)  resmux(aluout, readdata, memtoreg, result);
signext     se(instr[15:0], signimm);

// ALU logic
mux2 #(32)  srcbmux(writedata, signimm, alusrc, srcb);
alu         alu(srca, srcb, alucontrol, aluout, zero);
endmodule
```

MIPS Registerfile and Adder

```
module regfile(input clk, input we3, input [4:0] ra1, ra2, wa3, input [31:0] wd3, output [31:0] rd1, rd2);

    reg [31:0] rf[31:0];
    // three ported register file
    // read two ports combinatorially
    // write third port on rising edge of clk
    // register 0 hardwired to 0
    // note: for pipelined processor, write third port
    // on falling edge of clk

    always @(posedge clk)
        if (we3) rf[wa3] <= wd3;

    assign rd1 = (ra1 != 0) ? rf[ra1] : 0;
    assign rd2 = (ra2 != 0) ? rf[ra2] : 0;
endmodule
```

```
module adder(input [31:0] a, b, output [31:0] y);
    assign y = a + b;
endmodule
```

Shift-Left-2, Sign-Extension, Resettable Flip-flop, MUX2

```
module sl2(input [31:0] a, output [31:0] y);  
    // shift left by 2  
    assign y = {a[29:0], 2'b00};  
endmodule
```

```
module signext(input [15:0] a, output [31:0] y);  
    assign y = {{16{a[15]}}, a};  
endmodule
```

```
module flopr #(parameter WIDTH = 8)(input clk, reset,  
    input [WIDTH-1:0] d,  
    output [WIDTH-1:0] q);  
    always @(posedge clk, posedge reset)  
        if (reset) q <= 0;  
        else q <= d;  
endmodule
```

```
module mux2 #(parameter WIDTH = 8) (input [WIDTH-1:0] d0, d1,  
    input s, output [WIDTH-1:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```

Instruction Memory and Data Memory

```
module imem(input [5:0] a, output [31:0] rd);  
  reg [31:0] RAM[63:0];  
  
  // initial $readmemh("memfile.dat", RAM);  
  
  assign rd = RAM[a]; // word aligned  
endmodule
```

```
module dmem(input clk, we, input [31:0] a, wd, output [31:0] rd);  
  reg [31:0] RAM[63:0];  
  
  assign rd = RAM[a[31:2]]; // word aligned  
  always @(posedge clk)  
    if (we) RAM[a[31:2]] <= wd;  
endmodule
```

Top module

```
module top(input clk, reset, output [31:0] writedata, dataadr, output memwrite);  
  reg [31:0] pc, instr, readdata;  
  
  // instantiate processor and memories  
  mips mips(clk, reset, pc, instr, memwrite, dataadr, writedata, readdata);  
  imem imem(pc[7:2], instr);  
  dmem dmem(clk, memwrite, dataadr, writedata, readdata);  
  
endmodule
```

Esercizi

- Provare a descrivere in Verilog le reti combinatorie notevoli che abbiamo visto a lezione